

**Processor Description:** 8-bit single CPU with branch, jump, slt, sgt and function calls. A carry look-ahead adder for 8-bit inputs is also included.

**Features:**

Basic: ALU

Added: Support for SLT/SGT

Basic: R and I type

Added: Carry Look-Ahead Adder

Basic: LW and SW

Added: Branch-if-equal (beq)

Basic: Assembler

Added: Jump (j) Instructions

Basic: Writeup


Added : Support for function calls

## 1/ Assembler

Written in python, convert assembly code into hexadecimal machine language, each instruction is 14-bit long (the same as Lab4). The output file can be loaded directly to Logisim's instruction memory.

John's test 1

 add \$1 \$2 \$3 -> expected: 00000 001 010 011 = 53




Test on the reverse instruction (I use a simpler version of your test since my processor does not support intermediate number bigger than +3 and less than -4; it does the same job of switching data memory, I write this version so I can prove its correctness using my CPU.

<pre>#Reverse contents in data memory addi \$3 \$0 3 addi \$4 \$3 1 addi \$5 \$4 1  lw \$1 0 (\$0) lw \$2 0 (\$5) sw \$1 0 (\$5) sw \$2 0 (\$0)  lw \$1 1 (\$0) lw \$2 0 (\$4) sw \$1 0 (\$4) sw \$2 1 (\$0)  lw \$1 2 (\$0) lw \$2 3 (\$0) sw \$1 3 (\$3) sw \$2 2 (\$0)</pre>	<pre>20c3 2119 2161 2840 28a8 3068 3080 2841 28a0 3060 3081 2842 2883 305b 3082</pre>
---	---



## 2/ Basic 8-bit processor

- An 8-bit single cycle CPU with an ALU capable of addition, subtraction, and logical operations, supporting R-type, I-type, and load/store word from/to Data Memory.
- The processor uses 14-bit instruction and includes:
  - a register file with 8 registers.
  - a Program Counter (increment by 1 each time)
  - Instruction Memory (8-bit address width)
  - Data Memory (8-bit address width)
- Test the functionality of this processor using the hexadecimal translation from section 1:


Beginning State:

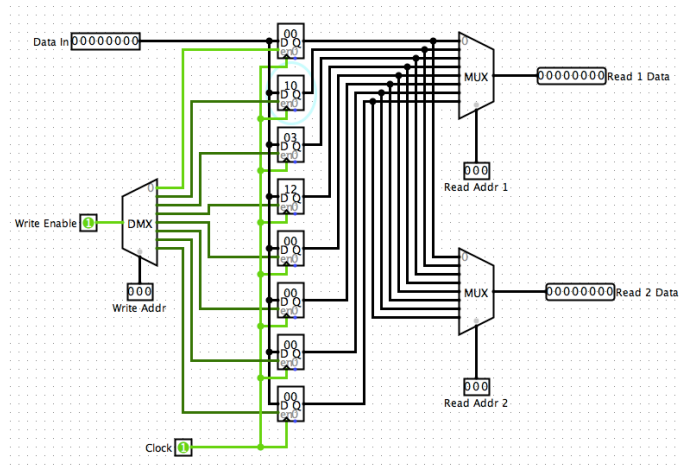

Instruction is fetched:

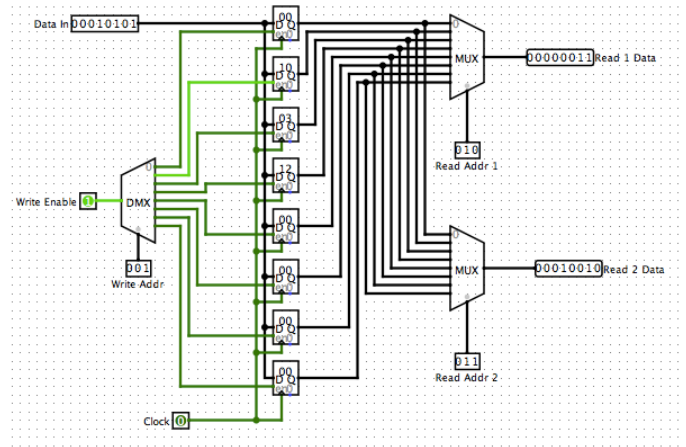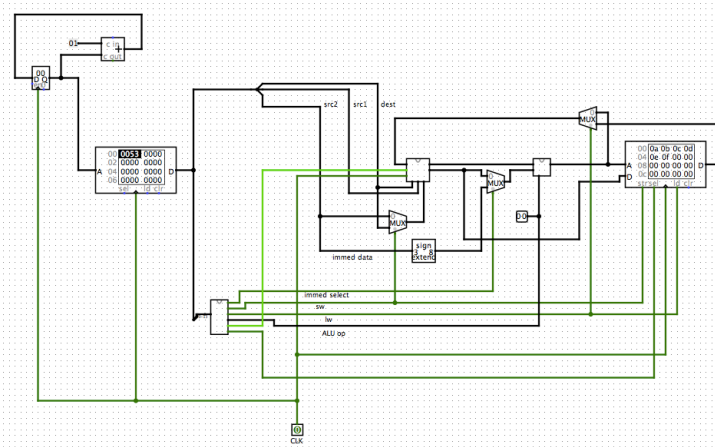


Final State:

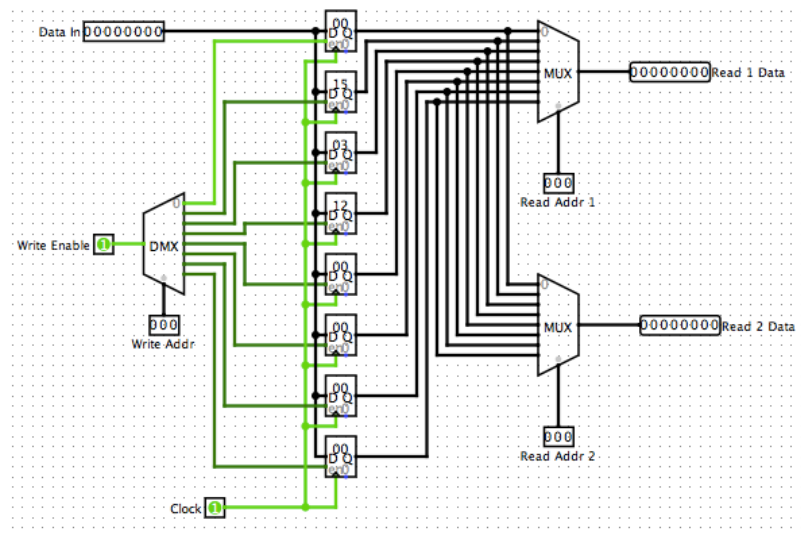

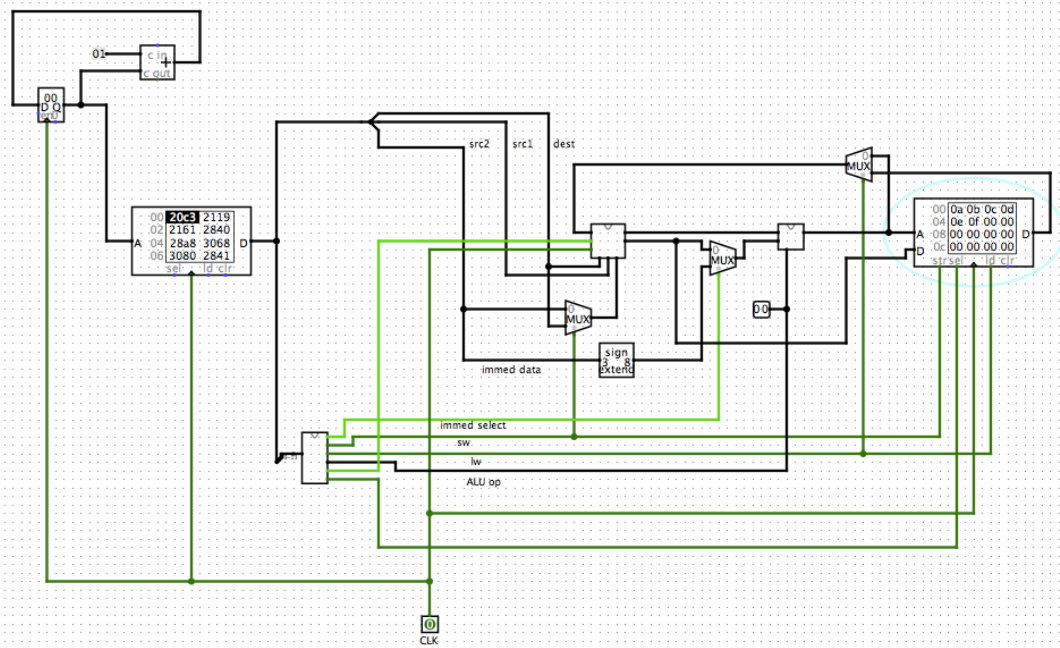
## Reverse:

- Beginning State (Data memory: 0a, 0b, 0c, 0d, 0e, 0f)




- Final State:

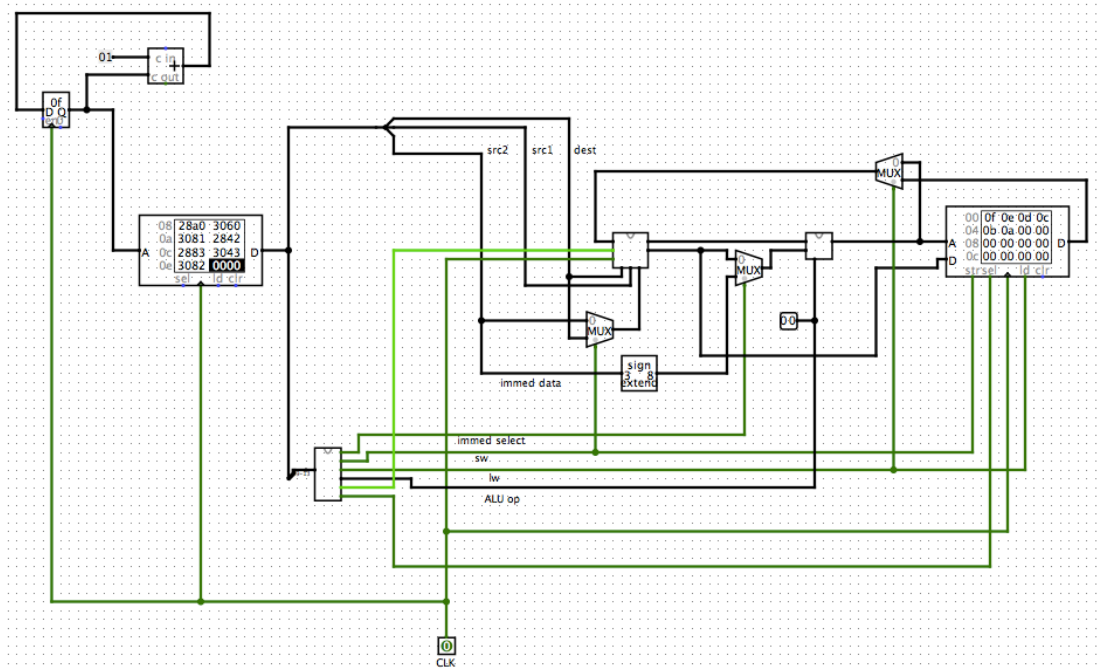
 
### Added Features:

- Here I use a 16-bit instruction, with 8-bit opcode (2 for jump/branch, 1 each for sw/lw/imm, 3 for alu operation).




### Instruction opcode:

Instruction	Branch (2-bit)	Intermediate (1-bit)	sw (1-bit)	lw (1-bit)	ALU-op (3-bit)
R-type: add	00	0	0	0	000
R-type: and	00	0	0	0	001
R-type: or	00	0	0	0	010
R-type: sub	00	0	0	0	011
R-type: slt	00	0	0	0	100
R-type: sgt	00	0	0	0	101
I-type: addi	00	1	0	0	000
I-type: lw	00	1	0	1	000
I-type: sw	00	1	1	0	000
R-type: beq	01	0	0	0	011
Jump: j	10	0	0	0	000
Jump-and-link: jal	10	0	0	1	000
Jump-return: jr	11	0	0	0	000



### 3/ SLT/SGT

- ALU operation, for two's complement


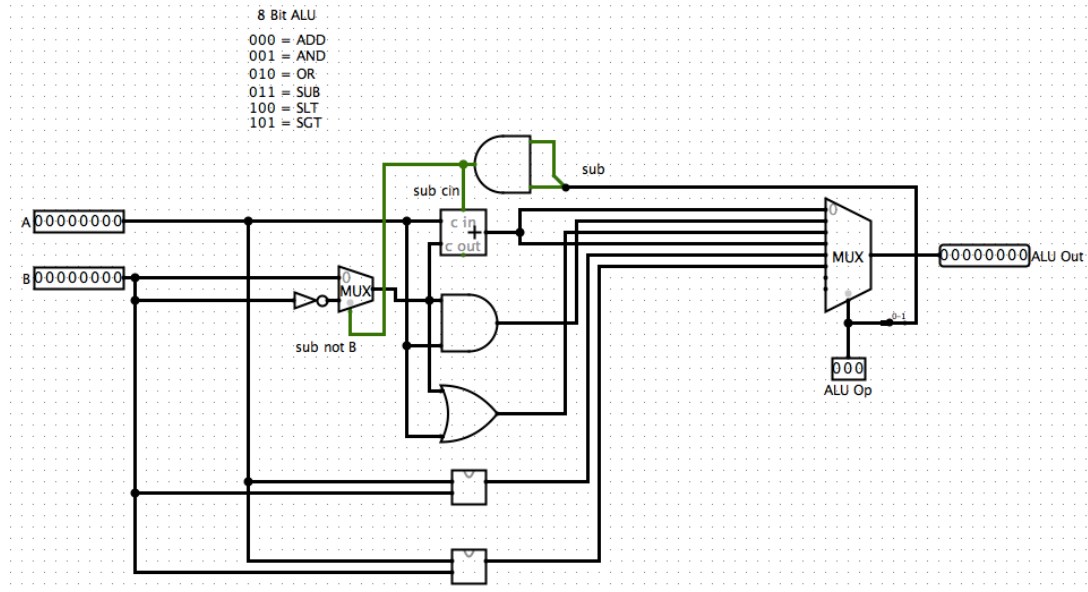


slt \$dest, \$reg1, \$reg2 will set \$dest to 1 if reg1 < reg2  
 sgt \$dest, \$reg1, \$reg2 will set \$dest to 1 if reg1 > reg2

- ALU test (slt)

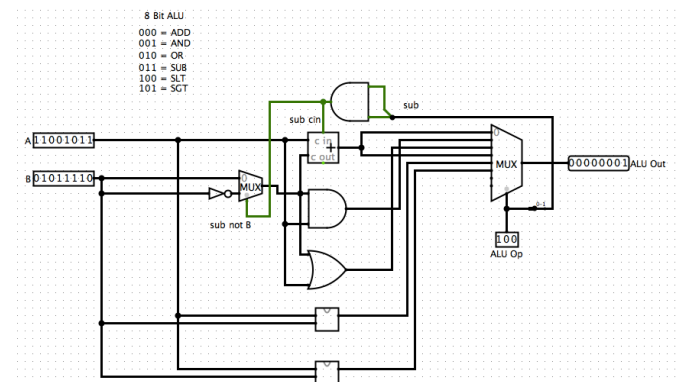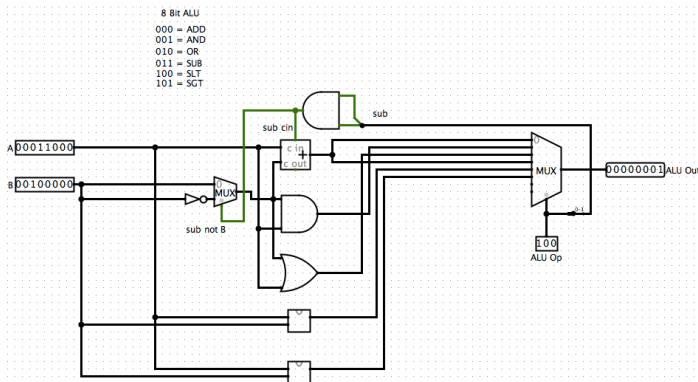

### ALU test (sgt)

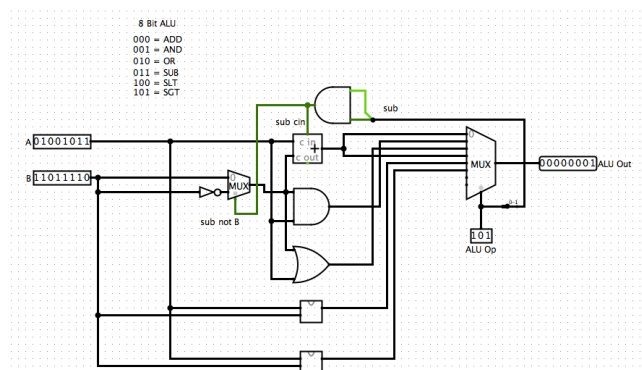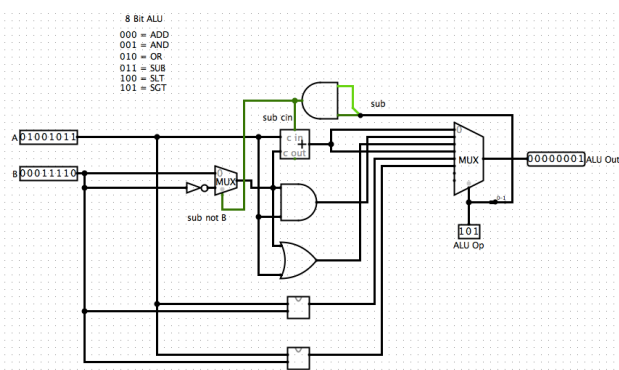

\$1 = 2; \$2 = -2; \$5 = \$6 = 1



True case: sgt \$3 \$1 \$0

slt \$4 \$2 \$0


False case: sgt \$5 \$0 \$1

slt \$6 \$0 \$2


Before:

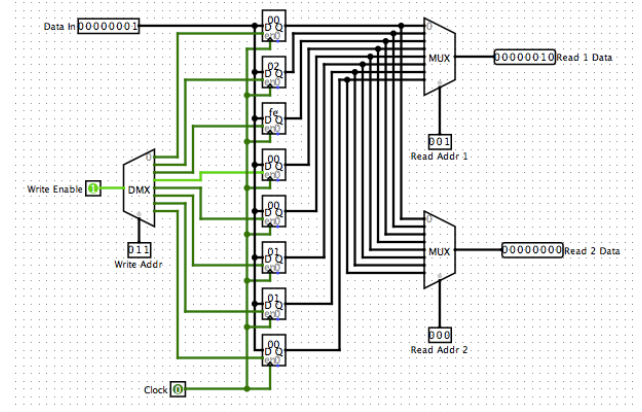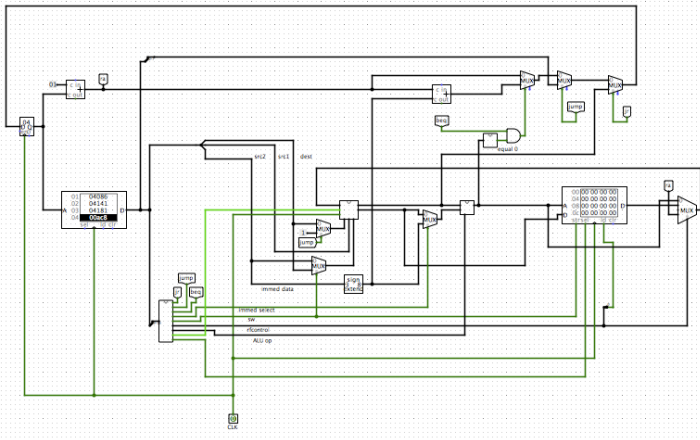

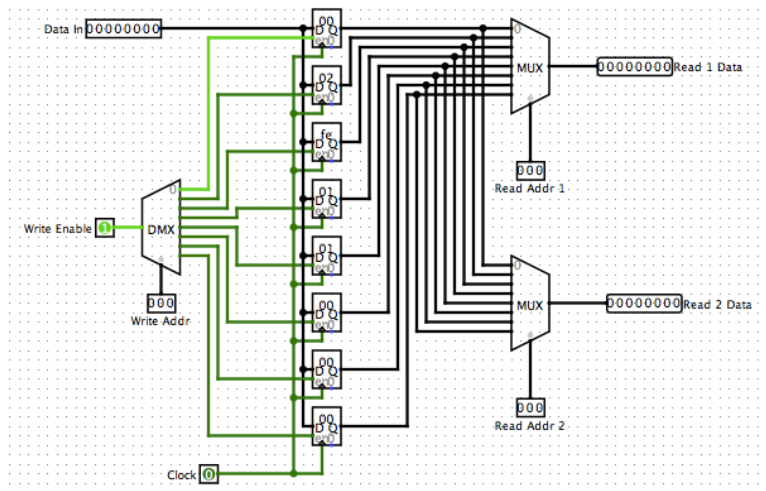After (value at \$3, \$4 change to 1; \$5, \$6 still 0)



#### 4/ Carry Look-ahead Adder:

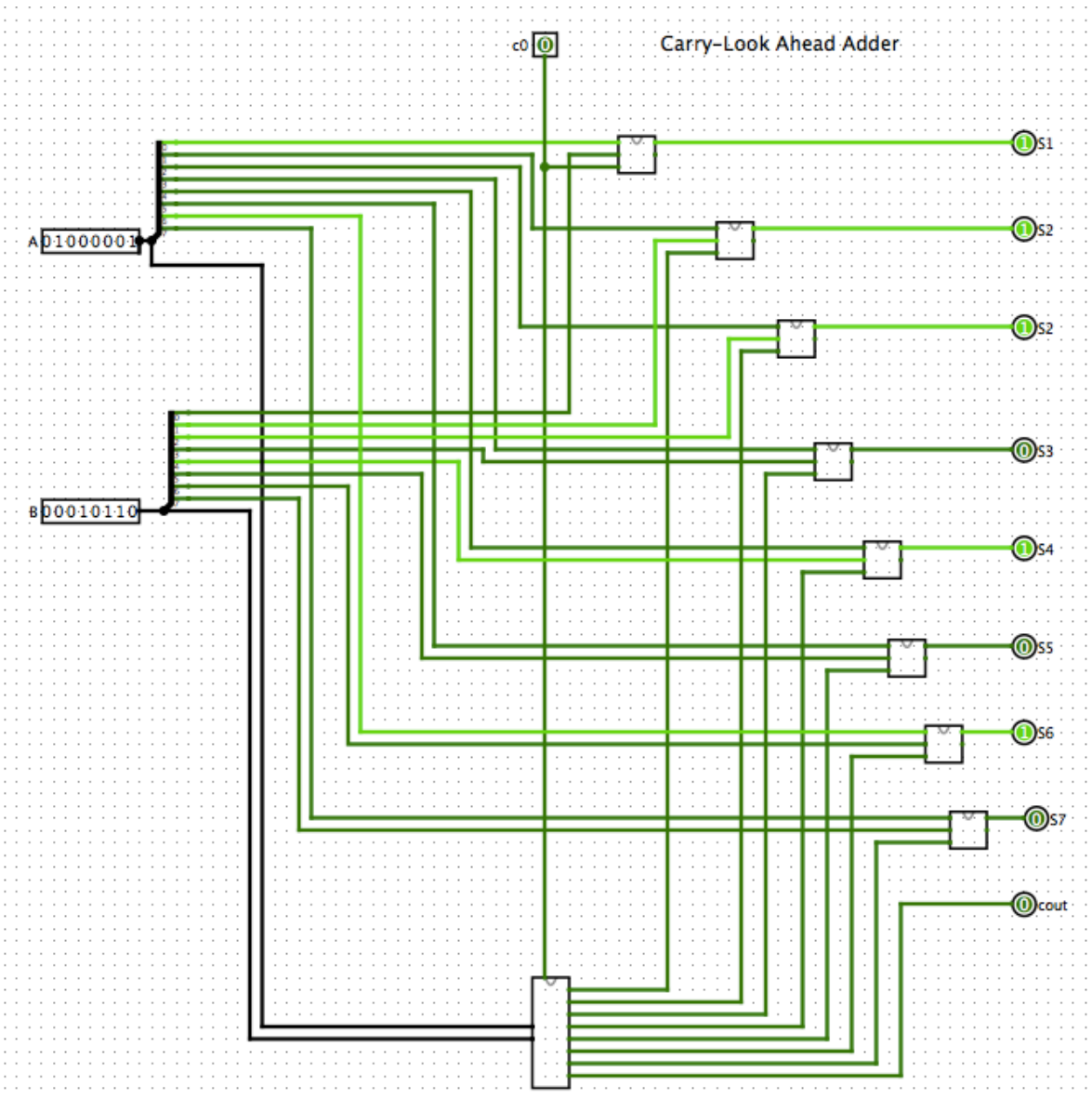





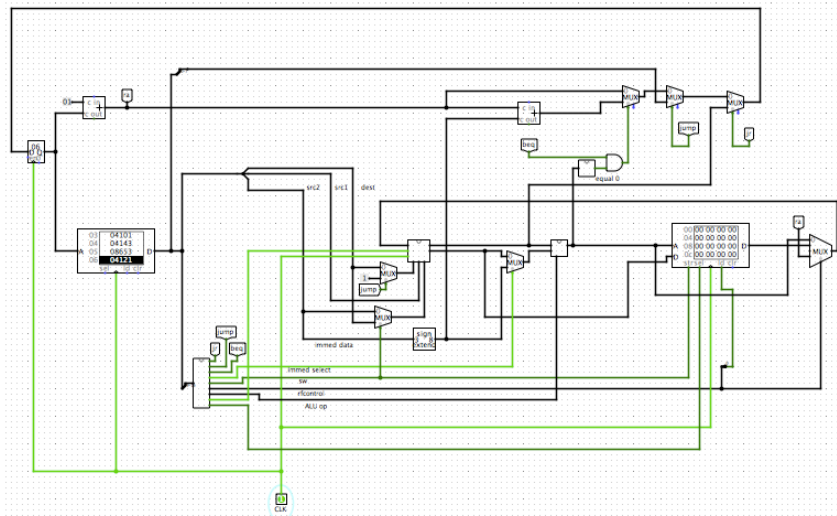
## 5/ Branch-if-equal (beq)

- Branch if reg1=reg2. The opcode is 01000011 (01 to specify beq and also ALU subtract op 011). Since my program counter only increments by 1 every clock cycle to move to the next instruction => just have to add the beq offset to pc. WE is disabled during beq instruction.
- John's test (I modified it to accommodate only the immediate value < 3)



The first branch (instruction #5) is not taken:



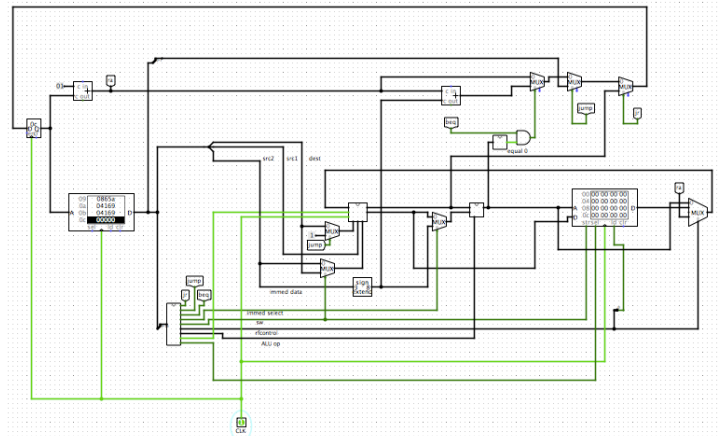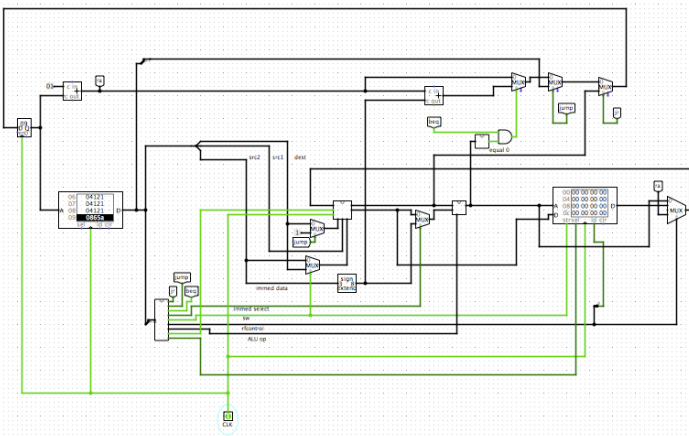
The second branch (instruction #9) is taken:



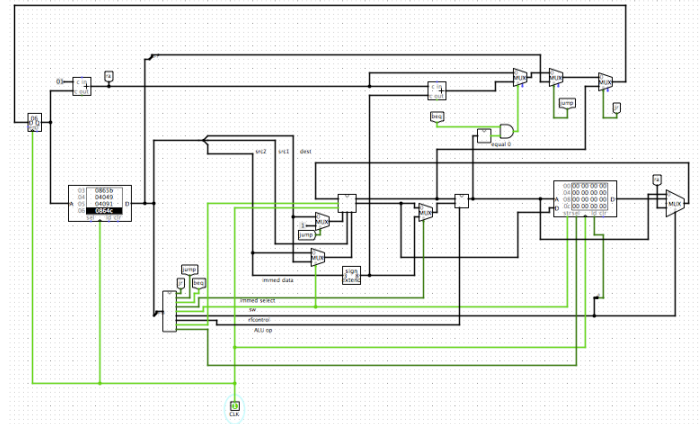 - First time: first branch is not take, second branch is taken





 First branch will be taken on the 3<sup>rd</sup> loop




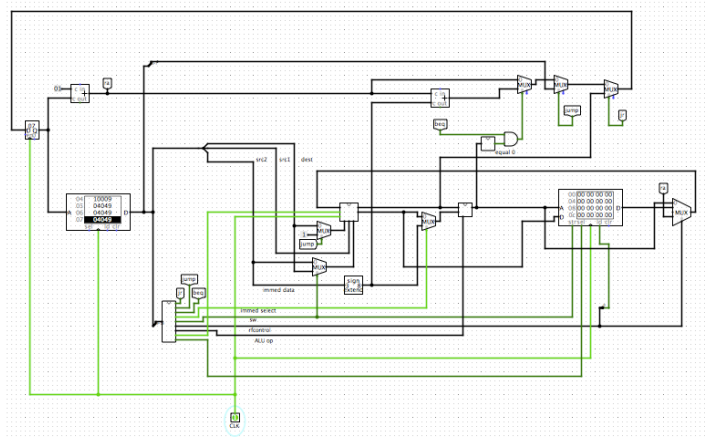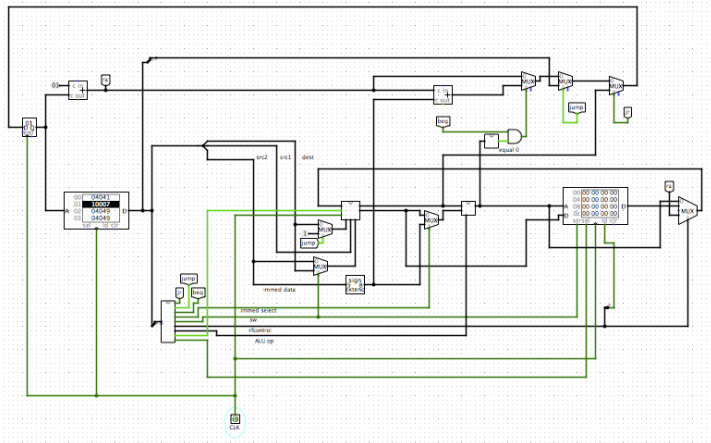
## 6/ Jump instruction:



- With 16-bit instruction and 8-bit opcode, the jump instruction is left with 9 bits to specify the address in instruction memory it wants the program to jump to. However, my instruction memory uses 8-bit address, thus, I decide that during jump instruction, my processor will only take into account bit 0-7 in the instruction when deciding which address to jump to. Since I have a much simpler cpu, I don't need to attach the region of the PC to my jump address.
- Test: first jump to address 7



Then at address 8 jump to address 3:

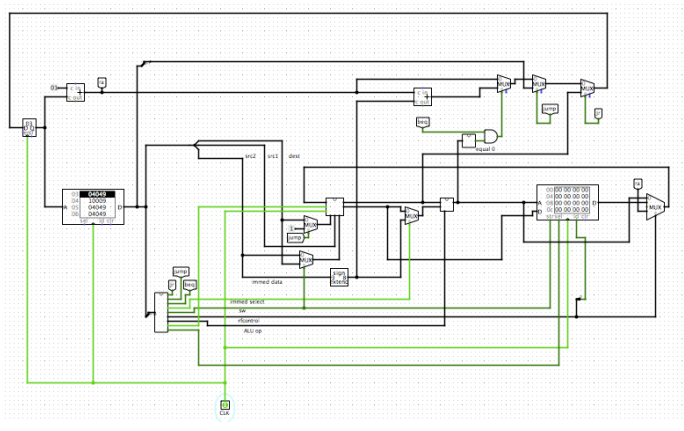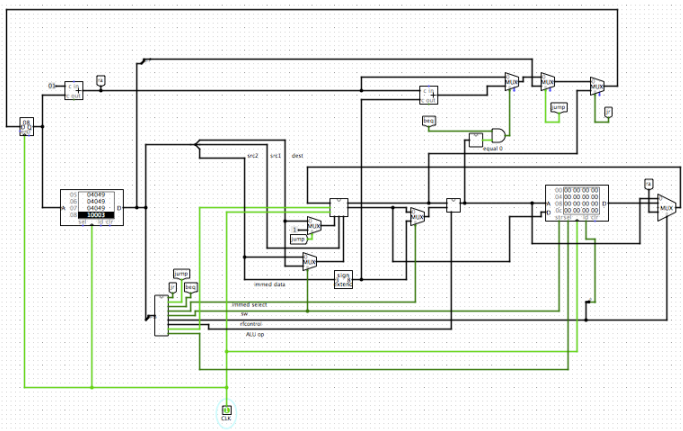



At address 4, jump out to address 9

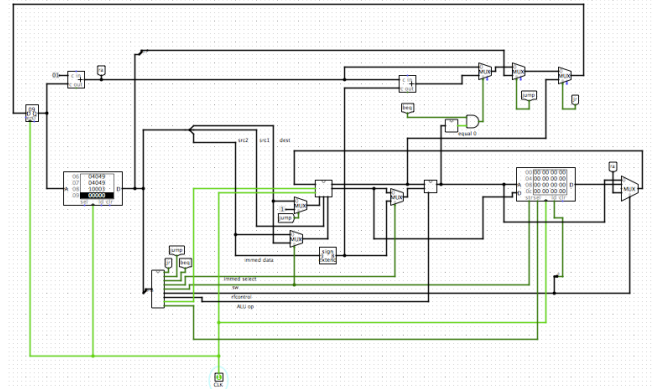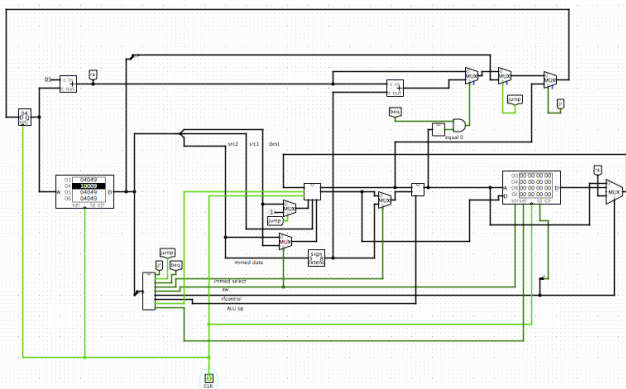



## 7/ Function call (JAL/JR)

- I only have 8 registers in my processor, thus, for function call I assume \$ra is always at register 1. Here I manually tested a very simple case where I jal to a random address (c0 in this case) and then jr back (at address c1).

### Beginning State (jal)

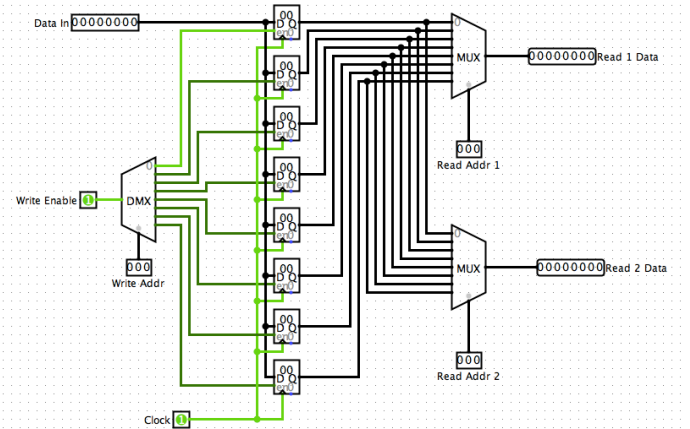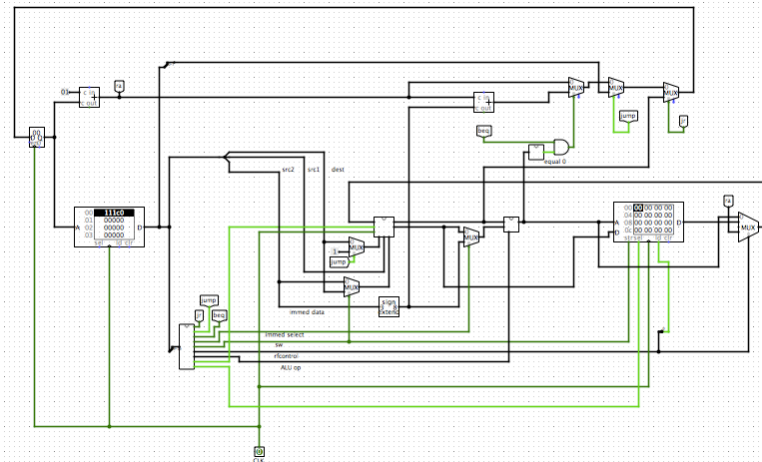

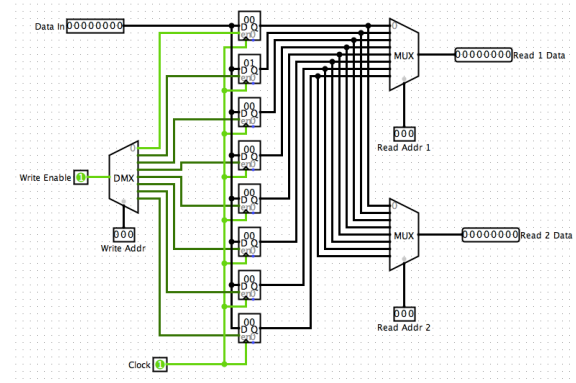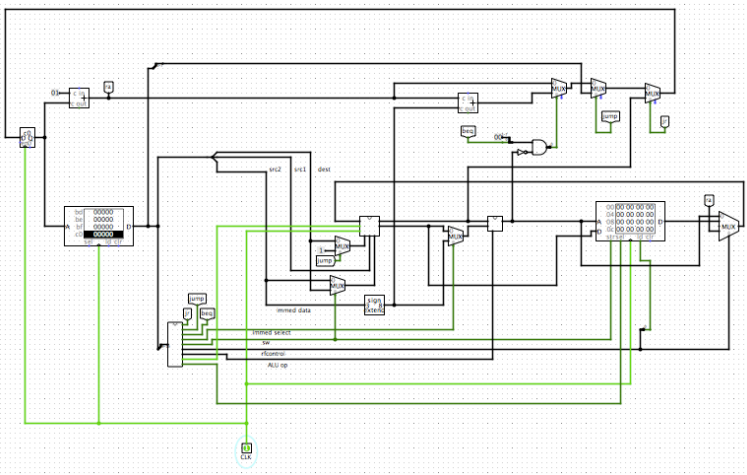After jal (PC jumps to new address, the return address (address 01 is stored in \$1)



Call jr \$ra (at address c1)

Beginning State:

